

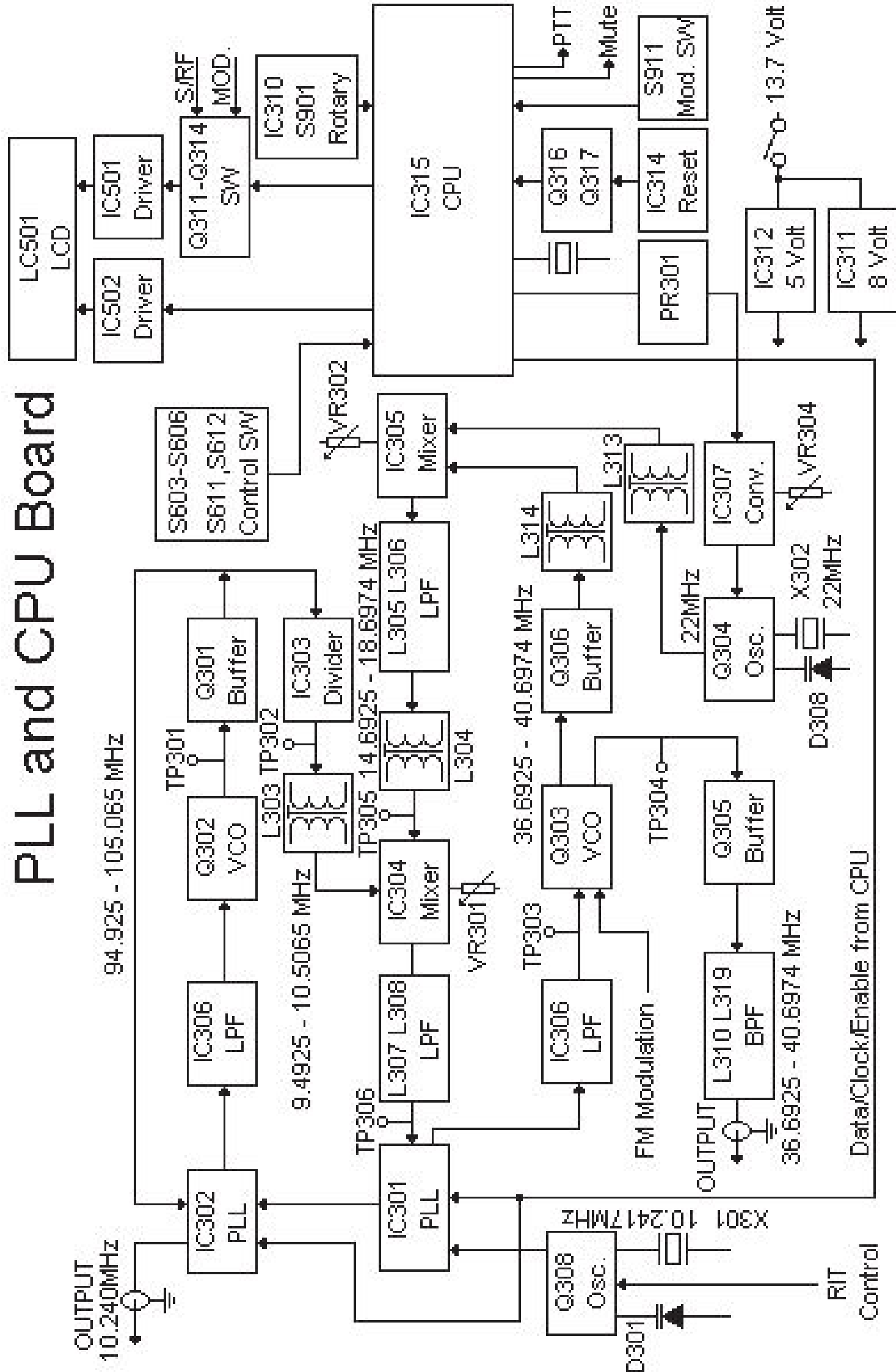


PLL and CPU Board

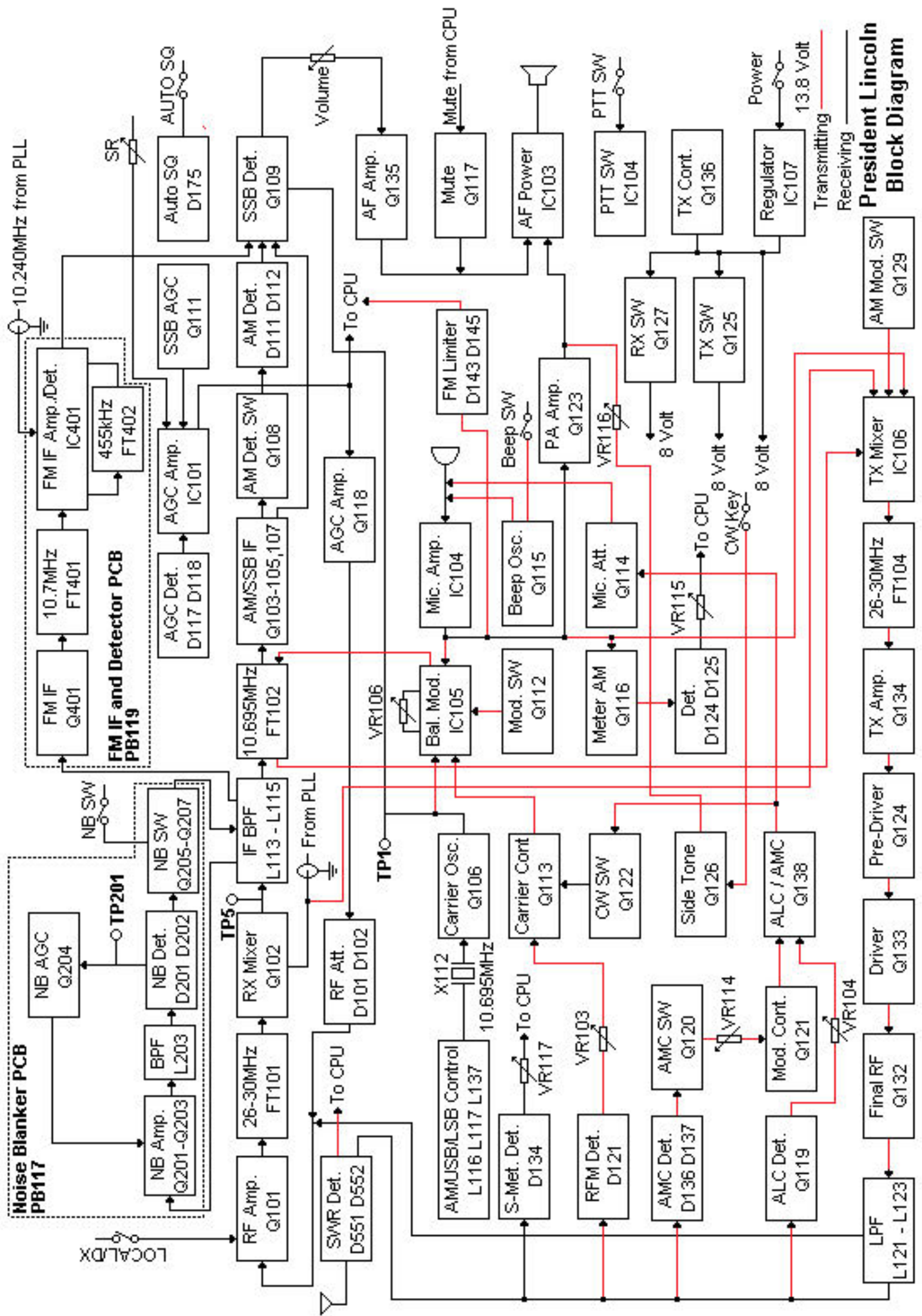

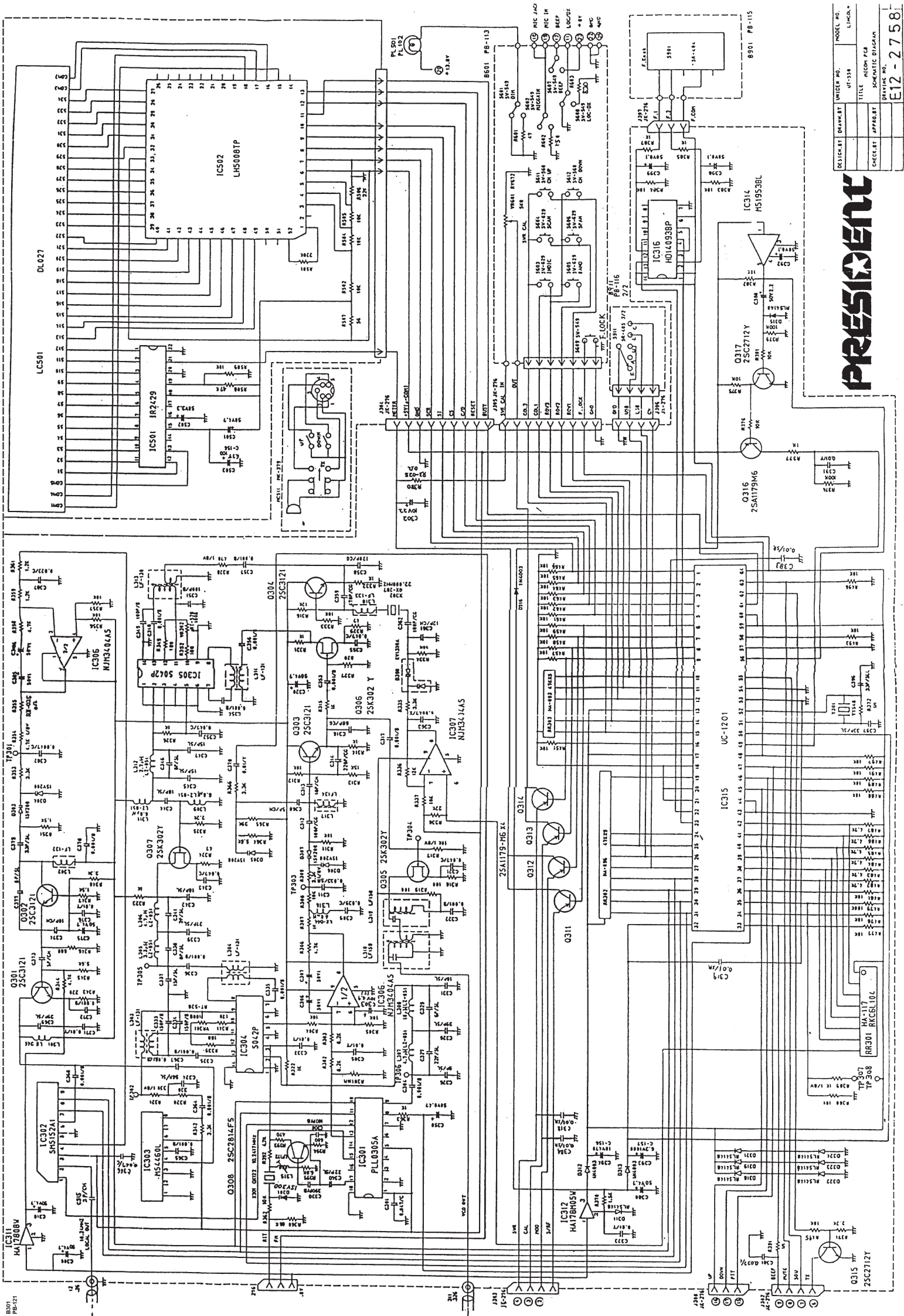


**President Lincoln
Block Diagram**





PRESIDENT

DESIGN-ET	DESIGN-ET	MODEL NO.	UT-334	LINCOLN
DRAWING	DRAWING	TITLE	SCHEMATIC	SCHEMATIC
CHECK-ET	CHECK-ET	APPROB-ET	APPROB-ET	APPROB-ET
DATE	DATE	DATE	DATE	DATE

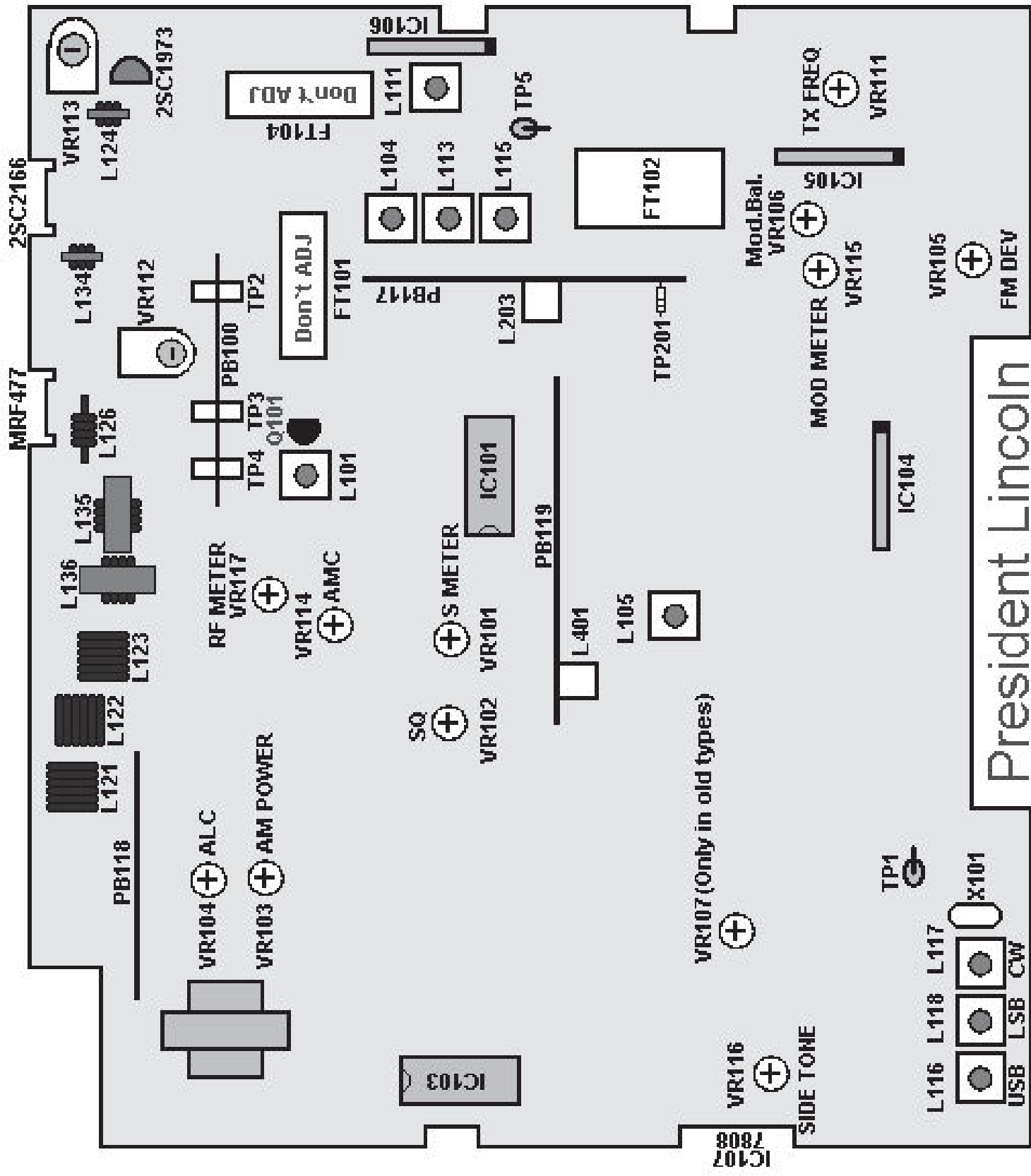


CPU and PLL Board

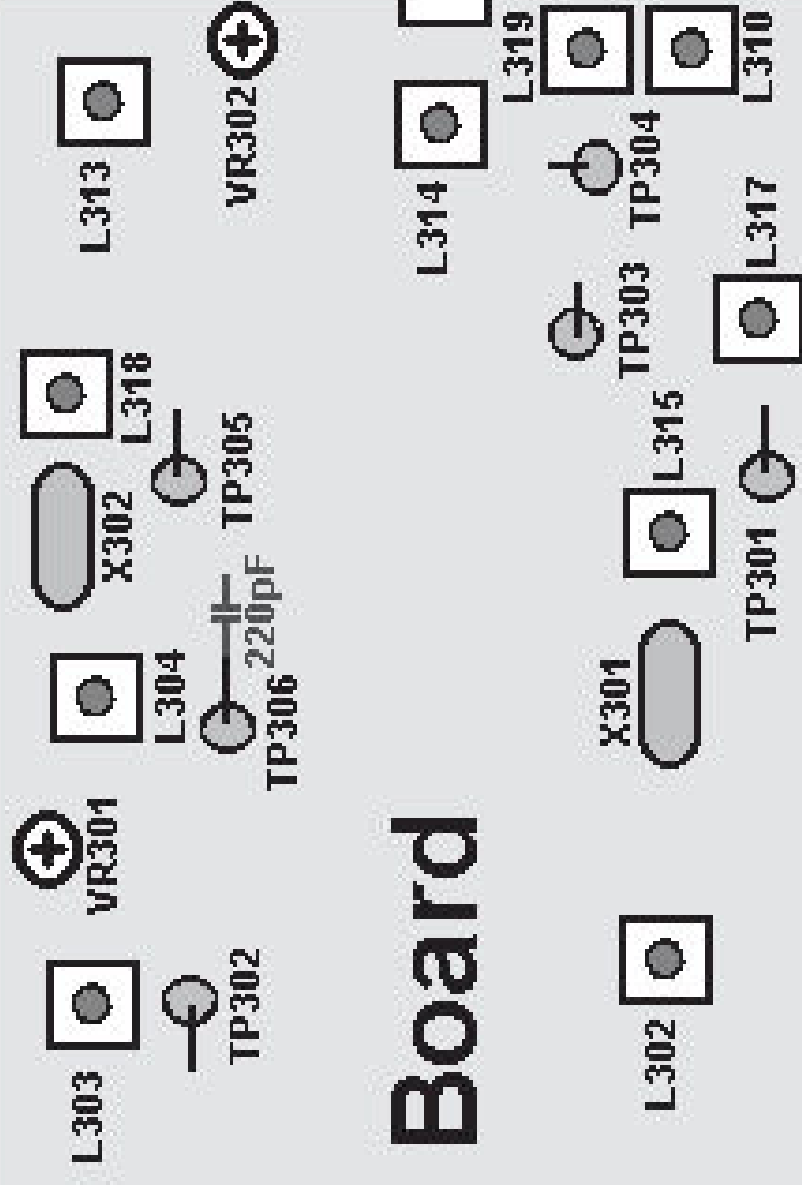

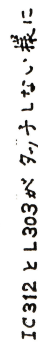


注意するにと

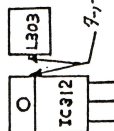
$$-7, \div NG$$

*.....BOGOT

IC311, 312 取付図

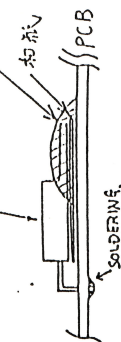

NOTES:

NOTES:
1. RESISTANCE VALUES ARE SHOWN IN OHMS UNLESS OTHERWISE NOTED. (K-KILO OHM, M-MEG OHM)
2. RESISTOR VOLTAGES ARE 1/6V UNLESS OTHERWISE NOTED.

※ L302・317・318・315は

調整後 パラフィンロックするにヒ.

DESIGN BY	DRAWN BY	UNIDEN NO.	MODEL NO.
83.3.18	63.3.9	UT-550Z	LINCOLN
CHECK BY	R. HAGA	TITLE	MICOM PCB
83.3.18	APPRO. BY	PARTS ASSEMBLY	TOP VIEW
		REV. MARK	
83.3.18		E23-7267	

通用
共使

UT-550A

C300	50V4.7	R304	10K	L301	LF246	IC301	PLL0305A	J301	JK276 3P
C302	10V22	R309	3.3K 1/8W	L302	LF132	IC302	SMS152AL	J302	JK276 4P
C303	10V4.7 1T1	R317	10K 1/8W	L303	LF131	IC303	MS4460L	J303	JK276 4P
C306	50V1	R321	330 1/8W	L304	LF131	IC304	5042P	J304	JK276 9P
C307	50V1	R323	1K	L305	LZ051 3.3P	IC305	5042P	J305	JK276 9P
C310	50V4.7	R328	470 1/8W	L306	LZ051 4.7P	IC306	NJM3404AS	J306	JK276 4P
C311	0.033(1SR)	R347	1.5K	L307	LZ051 4.7P	IC307	NJM3404AS	J307	JK276 4P
C320	50V4.7	R354	4.7K 1/8W	L308	LZ051 10P	IC311	HA17508W	J308	JK276 3P
C350	50V0.47	R356	10K	L309	LZ051 6.8P	IC312	HA178H05W	J311	JK326
C375	50V4.7	R365	39K	L310	LF159	IC314	MS19538L	J312	JK326
C380	50V4.7	R389	1K 1/8W	L311	LZ051 6.8P	IC315	UC1201		
C385	50V1			L312	LZ051 2.7P	IC316	HO140938		
C386	50V1			L313	LF130				
C388	50V2.2			L314	LF131				
C392	50V0.1			L315	LF172				
C393	6.3V1000 C-157			L316	LZ044 6.8P				
C394	10V470 C-156			L317	LF134				
C398	50V0.1			L318	LF133				
C399	50V0.1			L319	LF158				
C419	0.01 (5R)			X301	QX122				
					10.24(17MHz)				
				X302	QX287				
					22 0MHz				

PRESIDENT LINCOLN (HR 2510) MODS

by Roger Perales

<http://www.gj.net/~perales>



www.president.com

Downloaded from www.cbradio.nl

Table of Contents

To convert the HR2510 to 11 Meter operation:	4
To convert the Lincoln to 11 Meter operation:	5
HR2510 Modification for increased MicGain	6
President or Uniden HR-2510 Variable Power Modification	7
Increasing the power output for the HR2510	8
Modification of the HR2510 Mic buttons to operate the VFO	10
MOD # 1	10
MOD # 2	11
Talkback Removal.....	13
MOD #1 - The Relay Approach	13
MOD #2 - The Solid State Approach I	14
MOD #3 - The Solid State Approach II	15
HR2510 RIT / Clarifier Mods	16
RIT MOD I	16
RIT MOD II	16
RIT MOD III	16
RIT MOD IV	17
HR2510 Misc. Enhancements.	18
Increasing the Receive Audio I	18
Increasing the Receive Audio II	18
Increasing the Receive Audio III	18
Mute circuit improvement	18
Roger Beep Mods	18
Adding an external meter to the HR2510	19


If you are really interested, I suggest trying the CHIPSWITCH.	20
24 MHZ Broadband instructions for your HR2510	21
MOD #1	21
MOD #2 A simpler method... ..	22
HR2510 Alignment Instructions - (Taken from the Uniden Service Manual)	23
Alignment of P.L.L. and Carrier Oscillator Portion	23
Alignment of Transmitter Portion	24
Alignment of Receiver Portion	26
HR2510 Alignment and Test Point Layout	27
Synthesizer / Microprocessor / PLL PCB	27
Main PCB.....	27
HR2510 Circuit Block Diagram.....	29
Microphone wiring.....	29
Some interesting e-mails	31
Subject: Re: Kterou stanici vybrat ?	31
Subject: Re: Lincoln mods homepage	32
Subject: Mirror.....	32

To convert the HR2510 to 11 Meter operation:

Remove the cover on the speaker side of the radio. You will need to loosen the 4 screws (2 on each side) that secure the SYNTH PCB Frame to the chassi. - You do not need to remove these screws - You need to remove the 4 screws that secure the SYNTH PCB to the metal frame.

Now flip the SYNTH PCB over, Locate the pins of the Microprocessor. In some versions of the HR2510 there may be Grey Epoxy covering one end of the Microprocessor. You may be able to peel the epoxy right off to expose the pins of the IC. If it is not soft enough to peel off, you can use a 400W hair dryer to heat the epoxy enough to remove it.

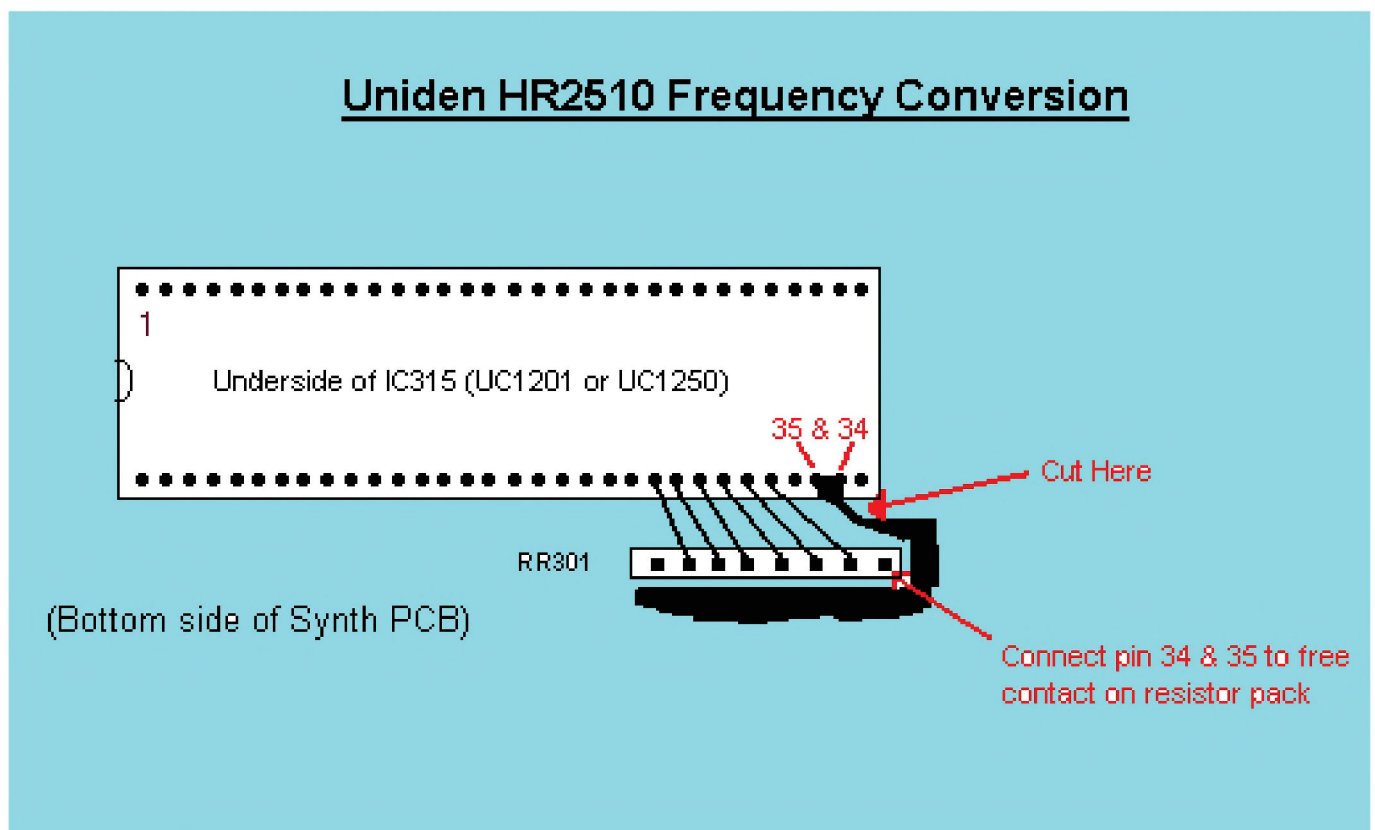Cut the ground trace connected to pins 34 & 35, jump pins 34 & 35 to the free end of Resistor pack RR301 (see diagram) or connect a 4.5K -15K ohm resistor from pins 34 & 35 to pin 3 of IC312 (5V



regulator).


This will give complete coverage from 26.000 MHz to 29.699 MHz (Some radios will go to 29.999 MHz)

To convert the Lincoln to 11 Meter operation:

Remove the cover on the speaker side of the radio..

Locate the the Microprocessor on the SYNTH PCB.

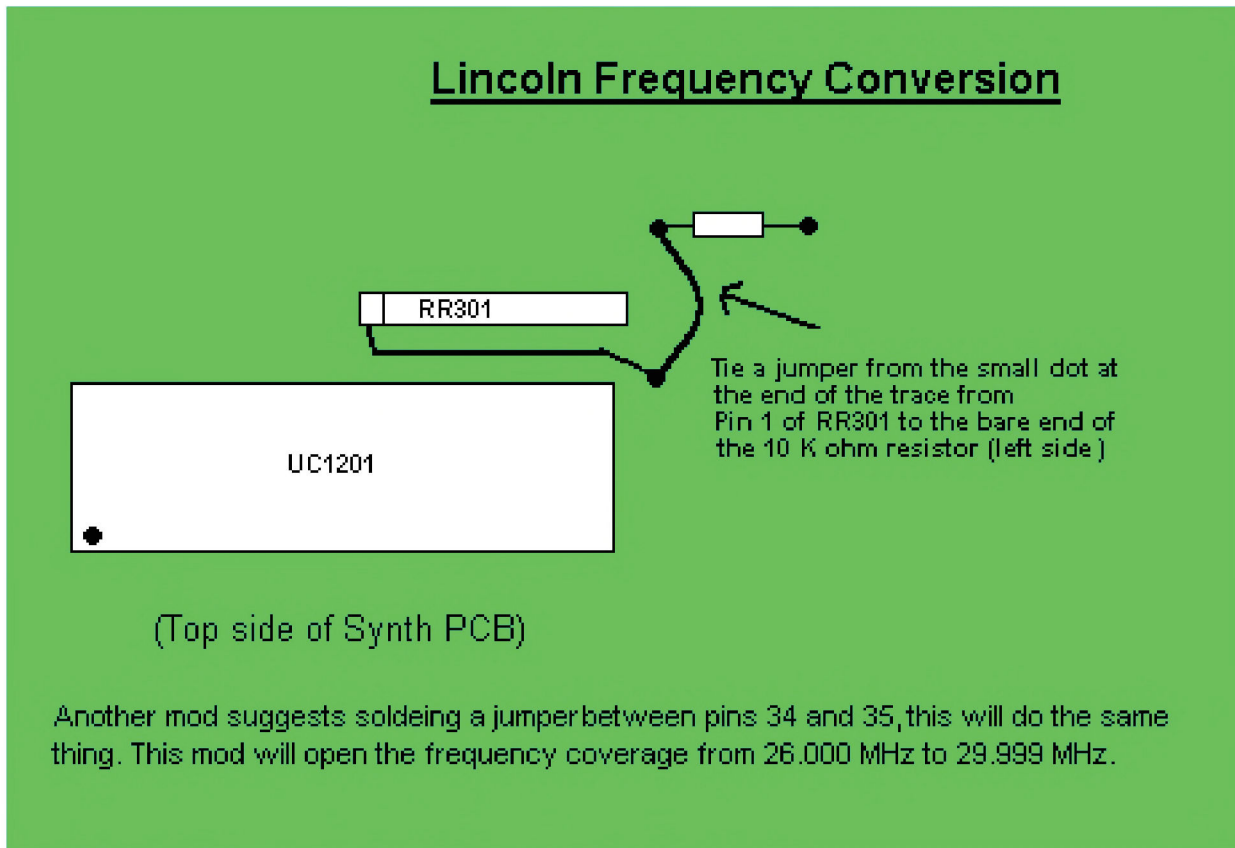Tie a jumper wire from the thru plate via hole at the end of the trace the bare end of the 10K ohm



Resistor. (see diagram) or connect pins 34 & 35 together..

HR2510 Modification for increased MicGain

This mod will increase the AM modulation.



The AM modulation adjustment is VR114, which is marked >AMC= on the main circuit board.

To get more, Q114 is the Mic Attenuator, This limits the audio.

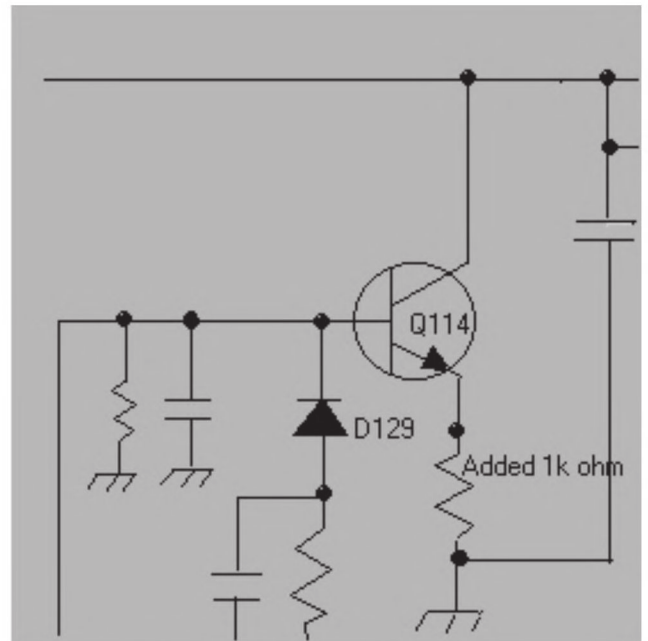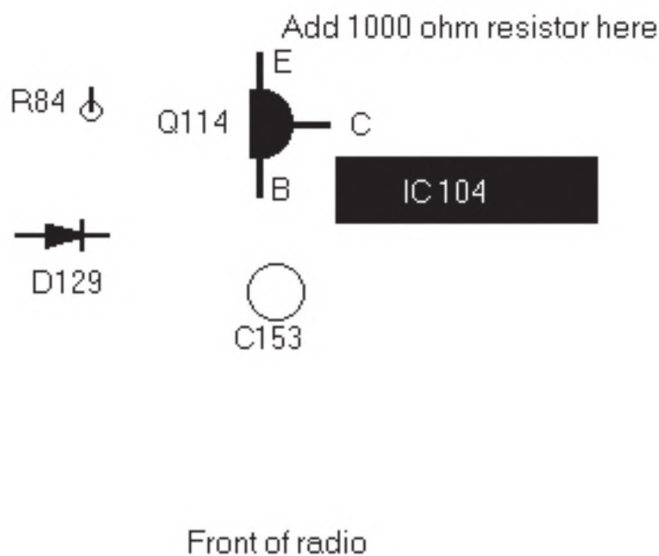Q114 is located near the front of the circuit board in the center to the left of IC 104, above C153.

To modify this, remove Q114 and bend the Emmitter leg up from the circuit board and re install.

Put a 1000 ohm resistor in the vacant hole and solder to the board.



Solder the other end of the resistor to the Emitter leg of Q114.

This will allow more modulation with the >stock= mic, and will allow a Power Mic to truly perform! The AMC control will still function so using a modulation meter you will be able to set it to avoid overmodulation.

Another Mod Suggests Clipping D129 to remove the ALC and AM limiting. I have heard from one user that this mod works exceptionally well.. I have not tried this mod, If anyone else has, please let me know the results.

Send E-Mail to rogerbird@juno.com

President or Uniden HR-2510 Variable Power Modification


The HR-2510 does not have a variable output power feature as it comes from the manufacturer. The following

Variable Power Mod for the HR 2510



Remove the White and Brown wires from the SWR CAL pot.
Connect a 4700 ohm resistor between the White wire and the brown wire, and Add a 4700 ohm resistor from the Brown wire to ground. (this allows the Meters to work properly).

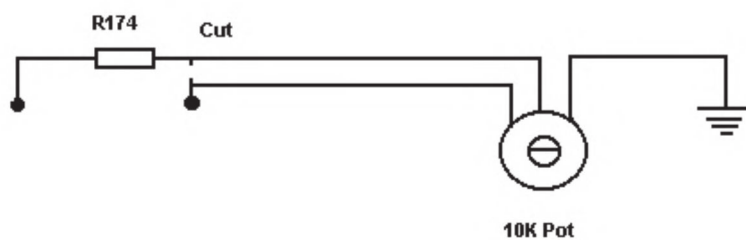Cut R174 on inside lead. wire from cut side of R174 to the left side of the SWR Cal pot.
Run a wire from the trace side of the cut R174 to the center of the SWR Cal pot.



modification will allow you to fix that oversight.

Increasing the power output for the HR2510


- 1). Remove the top and bottom covers.
- 2). Locate and remove Q132 & Q134.
- 3). Replace Q134 with an ECG 340 or TCG340.

WARNING!!! The leads of the two transistors are exactly opposite of each other.

[2SC2086 = BCE ; ECG340 = ECB.]

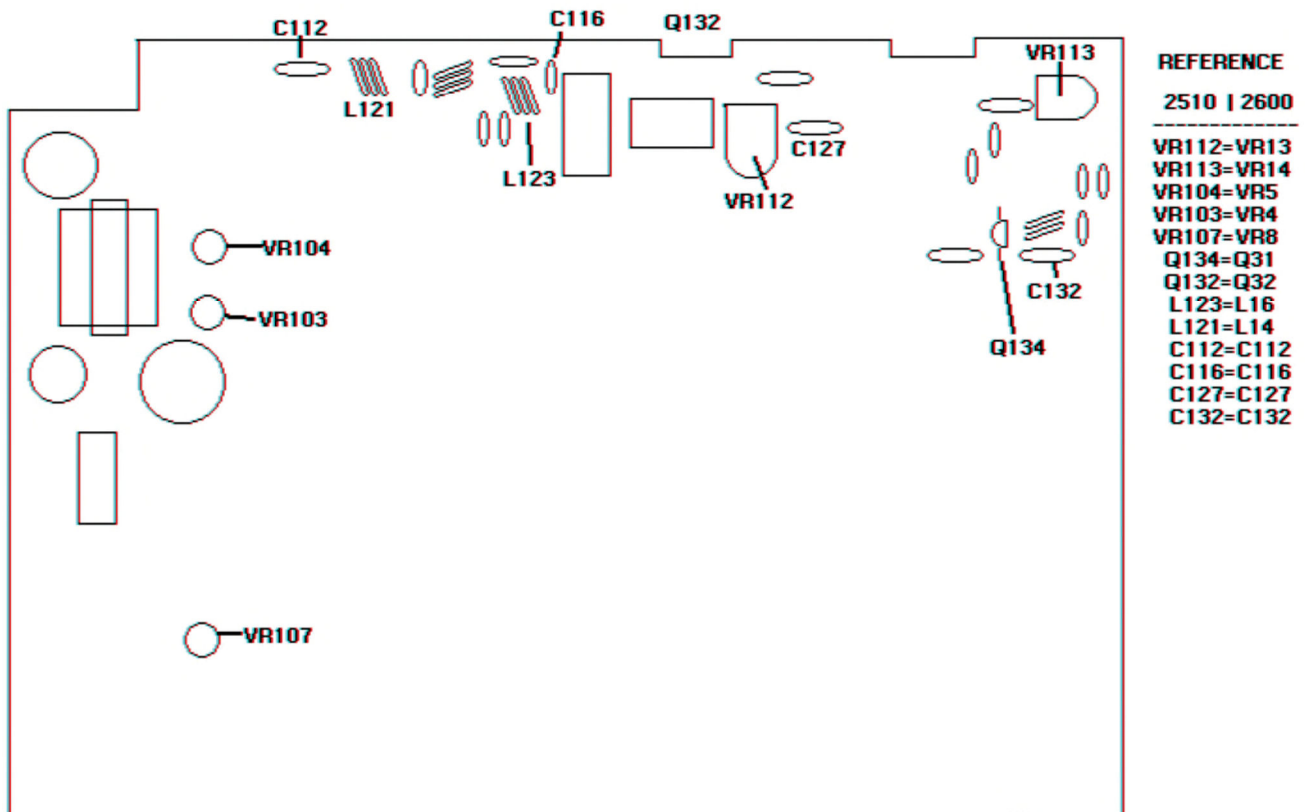- 4). Replace Q132 with an MRF 497. (Be sure to use heat sink compound.)
- 5). Remove C132. (no replacement)
- 6) Remove C112 & C116.
- 7). Replace C112 with an 82pf capacitor, But put the new Capacitor on the bottom of the PC board.
- 8). Replace C116 with an 100pf capacitor, But put the new Capacitor on the bottom of the PC board.

Component Layout with Cross reference for the HR2600



- 9). Connect power to the radio, and following the alignment procedures, adjust the bias of Q132 to 80mA +/- 5mA by adjusting VR112.

[To adjust the bias of Q132: Remove the B002(PB-100) jumper board from the Main PCB.

Connect a DC Ammeter (+) to TP4, (-) to TP3.

With the radio on USB, Adjust VR112 for 80mA +/- 5mA on the DC Ammeter.

After the adjustment is complete, Reinstall the B002(PB-100) jumper board.]

10). inject a two tone signal into the microphone of the radio while transmitting into a dummy load. Set VR104 (ALC) for maximum output..

Retune VR107 (AM /FM carrier level) for Maximum.

Retune VR103(CW carrier level) for Maximum

11). Again inject a two tone signal into the microphone of the radio while transmitting into a dummy load. Spread or contract coils L121 & L123 for the highest power out in the center of the band.

12). Replace the covers and the screws, you should now have between 50 and 100 watts on SSB.

This mod was originally written by M.T. Stacey, KC4HGH in an article published in CQ magazine of September 1989 on page 48. There was also supposed to be an Update in >73 magazine of November 1989 on page 76, Although I have never been able to find a copy to verify it.

Modification of the HR2510 Mic buttons to operate the VFO

Note: This modification is not needed if you have Chipswitched your radio already. The Chipswitch does this internally.

What these mods do is to disconnect the 5Khz steps and allow the Mic buttons to do what the Rotary switch does.



MOD # 1

The rotary switch applies 5 volts to activate the Up or Down control of the VFO. The Mic uses ground to activate the 5 KHz step control of the Up or Down buttons. The changes to the Mic are required because of these differences in the control operation.

The 1K resistor and 1N4001 diode combination causes the TX lead to be HI >5 volts= on receive and it protects the 5volt source on TX when the lead is grounded. (You must use a 1N4001 diode, because a 1N914 will not handle the current on TX).

Instructions:

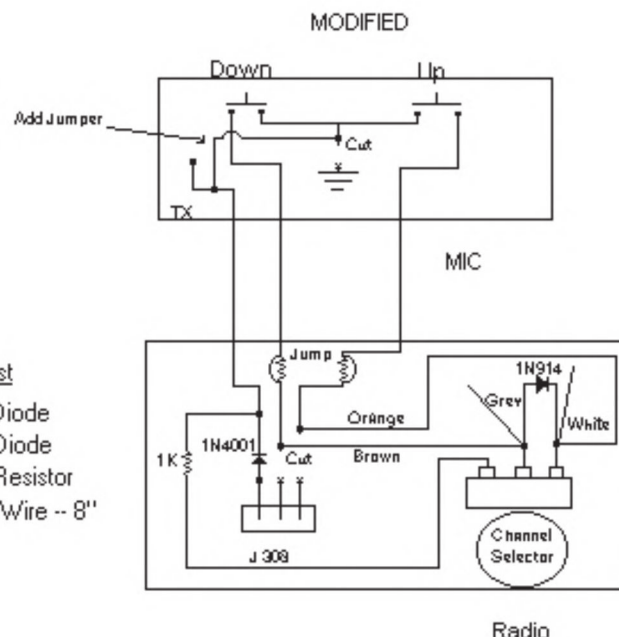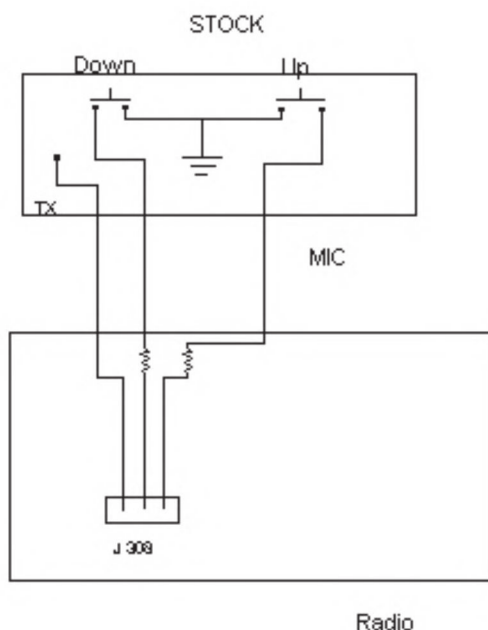- 1. Open the Mic and remove the ground from the Up and Down Switches and connect the common of the switches to the TX lead. (see diagram below) Reassemble the Mic.**
- 2. Remove both covers from the radio and look for the Mic jack. You will find 2 resistors, one on pin #4 and the other on pin #5. Jump out both resistors with wire.**
- 3. Find J308, located on the top left corner of the Microprocessor board. Cut the Yellow wire from the connector, leaving enough to attach a 1N4001 diode to each end, anode to J308 side cathode to the Mic jack. (see diagram below).**
- 4. Add a 1K ohm resistor to the cathode of the 1N4001 diode and wire the opposite end to the rotary switch, connect it to the etch on the back of the switch that does not have a Grey or White wire (Orange or Brown in the Lincoln) on it. Usually the Violet wire (usually Red in the Lincoln).**
- 5. Cut the Orange and Brown wires from J308 and route them to the rotary switch.**
- 6. Connect a 1N914 diode across across the Grey and White wires (Brown and Orange in the Lincoln) on the rotary switch. (see diagram below).**
- 7. Connect the Brown wire, cut from J308, to the White wire (Orange in the Lincoln) on the back of the rotary switch.**
- 8. Connect the Orange wire, cut from J308, to the Grey wire (Brown in the Lincoln) on the back of the rotary switch.**



Parts List
 1N914 --- Diode
 1N4001 --- Diode
 1K 1/4 W --- Resistor
 18 - 20 Gauge Wire -- 8"

NOTE: If the Up / Down buttons work backwards, exchange the Orange and Brown wires.

MOD # 2

Mod #2 is the same principal as Mod #1, But uses a Solid State approach, and does not require rewiring of the Microphone.

This Mod also allows for an automatic frequency increase or decrease as long as you hold the button down.

The rotary switch applies 5 volts to activate the Up or Down control of the VFO. The Mic uses ground to activate the 5 Khz step control of the Up or Down buttons.

Using a 4001 CMOS quad 2 input NOR gate, you can create a multivibrator to generate a pulsed output to allow the >automatic= function of the mod. The rest of the 4001s gates are used as gated inverters.

When the UP button is pressed it grounds pin 13, causing the pulse train on pin 12 to be outputted to pin 11 through the isolation resistor to the white wire on J307, this will increment the frequency of the selected digit on the HR2510, about 1 digit per pulse as long as the button is held down.

When the DOWN button is pressed it grounds pin 9, causing the pulse train on pin 8 to be outputted to pin 10 through the isolation resistor to the grey wire on J307, this will decrement the frequency of the selected digit on the HR2510, about 1 digit per pulse as long as the button is held down.


Instructions:

Refer to the Diagram below and create the circuit shown. You can use an experimenters perf board from Radio Shack (P/N 276-158A) and there is ample room in the HR2510 to mount it inside.

Hookup:


1. Connect the brown wire cut from J308 to the input pin 13 on the 4001 CMOS IC.
2. Connect the orange wire cut from J308 to the input pin 9 on the 4001 CMOS IC.

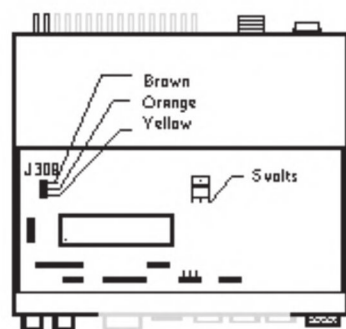3. Connect the output wire from the Isolation resistor on pin 11 of the 4001 CMOS IC to the top trace on the frequency knob. (the white wire).
4. Connect the output wire from the Isolation resistor on pin 10 of the 4001 CMOS IC to the 2nd trace from the top trace on the frequency knob. (the grey wire).
5. Connect the power wire to the 5 volt regulator pin 3 (facing the front of the radio, the far right leg of the L78MO5CV, located in the middle of the microprocessor circuit board). [see diagram]
6. Connect the ground wire to a good circuit ground.(you can use the left rear screw on the



PART LIST

QTY	Description
2	10 K ohm 1/4 Watt resistors
2	1 K ohm 1/4 Watt resistors
1	470 K ohm 1/4 Watt resistor
1	4.7 Megohm 1/4 Watt resistor
1	1N914 Diode
1	0.1 uf 50 volt capacitor
1	4001 CMOS IC

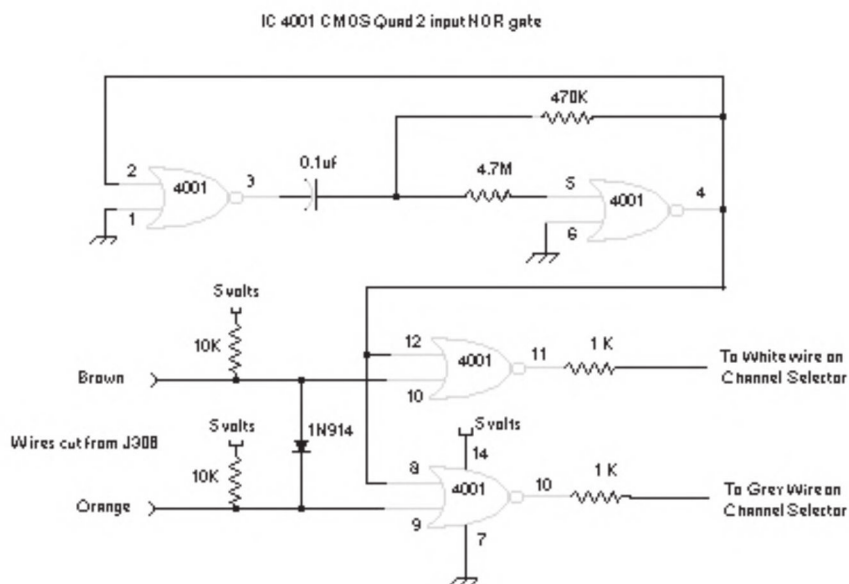

Based on an article by Carl Kollar (K3JML) in '73 magazine - Nov.1989

microprocessor board mounting).

After installation all the controls should work normally, and when pressing and holding the mic buttons the frequency should slide up or down the band at about 2 increments a second.

If you have any questions, you can E-mail me. Although I have not tried this mod (MOD #2) it is fairly straight forward.

Talkback Removal

MOD #1 - The Relay Approach

One method of Talkback removal is to break the speaker line with a relay.

Parts needed :

12Volt SPDT relay

2 - 1N4148 Diodes

1 - 1N 4001 Diode


Several pieces of hookup wire

Jumper the Relay coil - K1 with a 1N4001 Diode - D1. To key the relay you connect one side of the Relay coil (the side with the Cathode of the diode) to IC107 pin 1.(HA17808W)

Cut the Blue wire that goes to pin 1 of the AUX plug on the rear of the radio. (Make sure you leave enough wire to reconnect each end to wires for the relay.) Attach the wire from pin 1 of the AUX plug to the Wiper contact of the Relay- K1. Attach the other half of the Blue wire to the Normally Closed side of the Relay.

(Make sure you leave enough wire to reconnect each end to wires for the relay.)

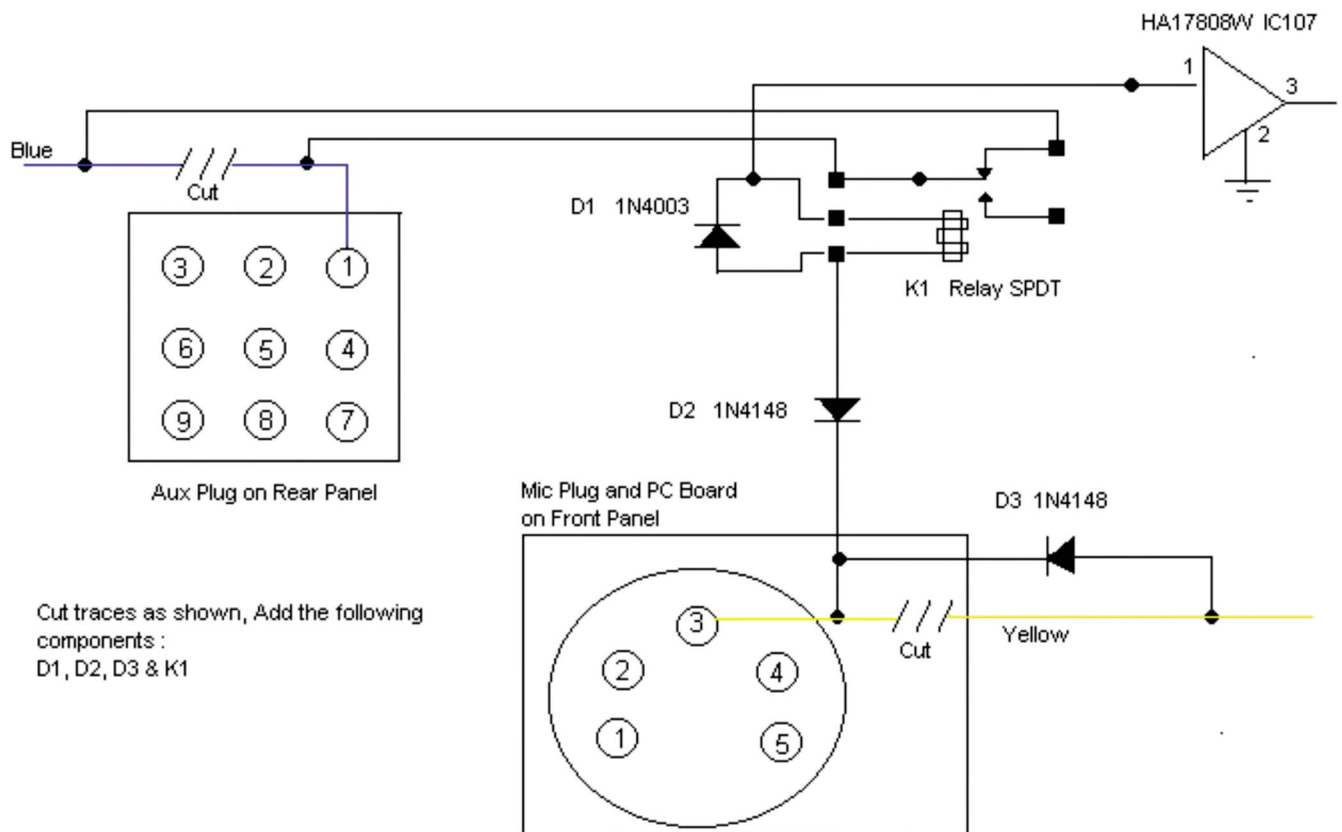Cut the Yellow wire from pin 3 of the Mic plug. Jumper the cut Yellow wire with a 1N4148 Diode - D2 (Cathode to the Mic Plug Pin 3) Connect the last 1N 4148 Diode - D3 to the Relay coil, Anode side to the Anode of the Diode - D1 on the coil of the relay. Connect the Cathode to Pin 3 of the Mic plug.(Cathode to Cathode of the two diodes on pin 3 of the Mic plug.)




MOD #2 - The Solid State Approach I


All that is needed is to add a 1N914 Diode from pin 6 of IC103 to the collector of Q125.

Connect the cathode of the diode to pin 6 of IC103, and the anode to the collector (the center pin) of Q125.

TALKBACK ELIMINATION MOD 2

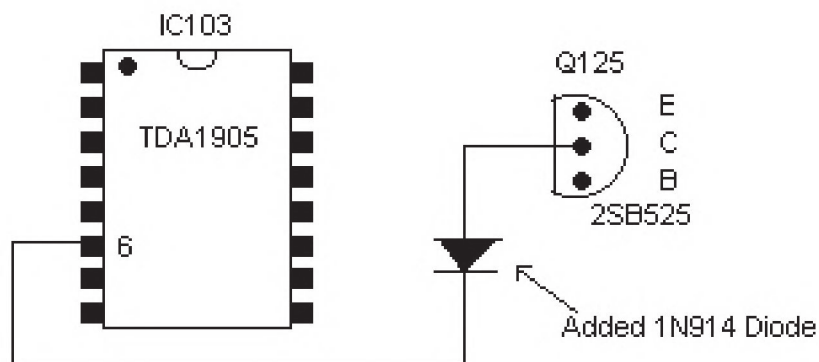

TALKBACK ELIMINATION MOD 3

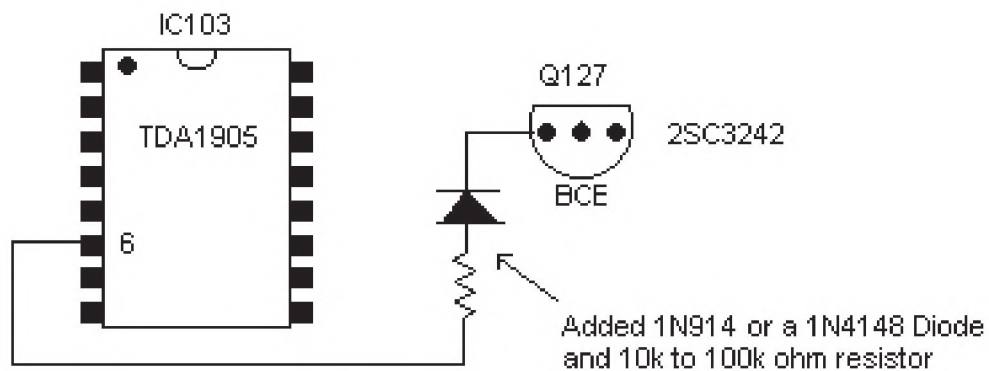

NOTE: Use a 10k ohm resistor if you only use the internal speaker.
Use a 100k ohm resistor if you use a external speaker.

MOD #3 - The Solid State Approach II

All that is needed is to add a 1N914 or a 1N4148 Diode connected to a 10k to 100k resistor from pin 6 of IC103 to the Base of Q127.

Connect the anode of the diode to one side of the resistor. Connect the other side of the resistor to pin 6 of IC103, and the cathode to the Base of Q127.

Note: Use a 10k ohm resistor if you only use the internal speaker. Use a 100k ohm resistor if you use an external speaker.

These last 2 MODs remedies the Audio Feedback caused by the Audio Amplifier chip, IC103 (TDA 1905) not being switched over completely from RX to TX when you key the mike. These fixes rebias the switching transistor to correct this.

HR2510 RIT / Clarifier Mods

The RIT (Receiver Incremental Tuning) on the HR2510 is a Clarifier control to help >tune in= usually SSB signals that may be transmitted off of center. The RIT only works on the receiver. The HR2510 does not allow >slide= on transmit unless its modified. Many people wish to >Open= the RIT (or Clarifier).

Everyone has a different mod for this one, I will list the ones I know. Basically they are about the same, You need to disconnect the existing voltage from the clarifier (RIT) circuit and add a constant voltage to the clarifier (RIT) control circuit.

This voltage needs to be there during transmit.

RIT MOD I

Find D150 on the main circuit board. With the radio right side up, it will be found in the front right-hand corner of the PCB.

Lift or clip one end of this diode.

Find the orange wire coming from the RIT/RF GAIN PCB (PB-120). From there it goes to the main PCB to a 4 wire connector (Yellow/Orange/Red/Brown) located on the left side of the main PCB near the center of the radio. Clip the orange wire from the connector and feed it through to the other side of the radio. Solder it to pin 3 of IC 311. This will be a three-pin voltage regulator located just to the right of the large microprocessor (IC315). The pins on IC 311 are numbered from left to right.

To center the RIT:

Locate the 3 tuning coils on the front left corner of the main PCB. The extreme left coil labeled L116, adjusts USB. The center coil is labeled L118, adjusts LSB. The right coil labeled L117, adjusts CW. There will be some interaction between the coil adjustments so you may need to repeat retuning a few times. I suggest you start with the USB coil and end with the CW coil.

The Mod will give you plus or minus 3 Khz slide, the RIT will NOT change the display, but the transmit and receive frequency will track together now.

RIT MOD II

Cut D150 on the main PCB. Locate the orange wire at the top of the RIT PCB, cut and connect to pin 3 of IC107. This is a 3 pin transistor bolted to the left side of the case next to VR116. Pin 3 is the lead closest to the back of the radio. You now have +/- 5khz slide.

RIT MOD III

Find the orange wire coming from the RIT/RF GAIN PCB (PB-120). From there it goes to the main PCB to a 4 wire connector (Yellow/Orange/Red/Brown) located on the left side of the main PCB near the center of the radio. Clip the orange wire from the connector. Find the red wire (8 Volts) on the mode switch PCB and solder the orange wire to it.

To Adjust:

Set the RIT to center (12 o'clock) Mode switch to AM Frequency to 28.000 Mhz.

Connect a Frequency counter to TP306. Adjust L315 for 6.200Mhz

Connect a Frequency counter to TP304. Adjust L318 for 38.695Mhz

Connect a frequency counter to TP1.

Set the Mode switch to USB, adjust L116 for 10.6975Mhz.

Set the Mode switch to LSB, adjust L118 for 10.6925Mhz

Set the Mode switch to CW, adjust L117 for 10.6950Mhz

Check RIT range. It should be +/- 4Khz

RIT MOD IV

Find the orange wire coming from the RIT/RF GAIN PCB (PB-120). From there it goes to the main PCB to a 4 wire connector (Yellow/Orange/Red/Brown) located on the left side of the main PCB near the center of the radio. Clip the orange wire from the connector. Solder the orange wire to Jumper 13 (JP13) +8V constant . Cut D150.

To center the RIT: With the Mode switch to AM, Frequency at 28.000Mhz, RIT at 12 o'clock, connect a frequency counter to TP304, adjust L318 for 38.695Mhz.

HR2600 NOTE:

D150 is for the HR2510, D43 is for the HR2600, also in the HR2600 the wire may be orange or brown. The

connector on the main PCB is a 5 wire connector.

HR2510 Misc. Enhancements.

Increasing the Receive Audio I

The HR2510 does not have a by-passed emitter in the audio circuit. To correct this, Add a 4.7uf 16v Electrolytic capacitor across (in Parallel) with R152 (a 560 ohm resistor). This modification will increase the receive audio.

Increasing the Receive Audio II

This mod will increase the AM reception: Replace the AM Detector diodes (D111 & D112) with better Schottky Barrier diodes. You can use ECG 583 or NTE 583 diodes or 1N6263 or equivalent. (In the HR2600 the diodes are labelled D11 & D12).

Increasing the Receive Audio III

This mod will increase receive strength and dynamic range, resulting in louder, cleaner signals while actually reducing noise levels. All you need to do is to replace the existing IF Amp transistor with a new one which has greater frequency response and lower noise characteristics. Once installed you will need to adjust your AS@ meter for more realistic readings.

1.) Remove diode D101 and Transistor Q101.

2.) Replace Q101 with a ECG or NTE 23.

NOTE: The new transistor has a different pin out from the original. You will need to reorient the new transistor to work. With the flat side of the transistor facing you and leads pointing down : Existing leads of Q101 = 1 2 3 , the replacement ECG or NTE, you will need to cross the first lead to the last = 2 3 1 .

Mute circuit improvement

To Improve the operation of the Mute circuit, remove C139 and R199. These two components are connected to the base of Q117.

Roger Beep Mods


The Roger Beep in the HR2510 is >Unique= but kind of wimpy..To modify this, locate R96 (a 2.7 Meg. ohm resistor).

Remove and replace with a 100K ohm 1/8 watt resistor. This will increase the amplitude of the beep.

To change the duration (length) of the beep, replace C110 (10uf 16v) remove and replace with a capacitor at least 50v with more or less capacitance to lengthen or shorten the beep to your preference.

These components are located to the left (facing the front of the radio) of IC 104.

Component location diagram

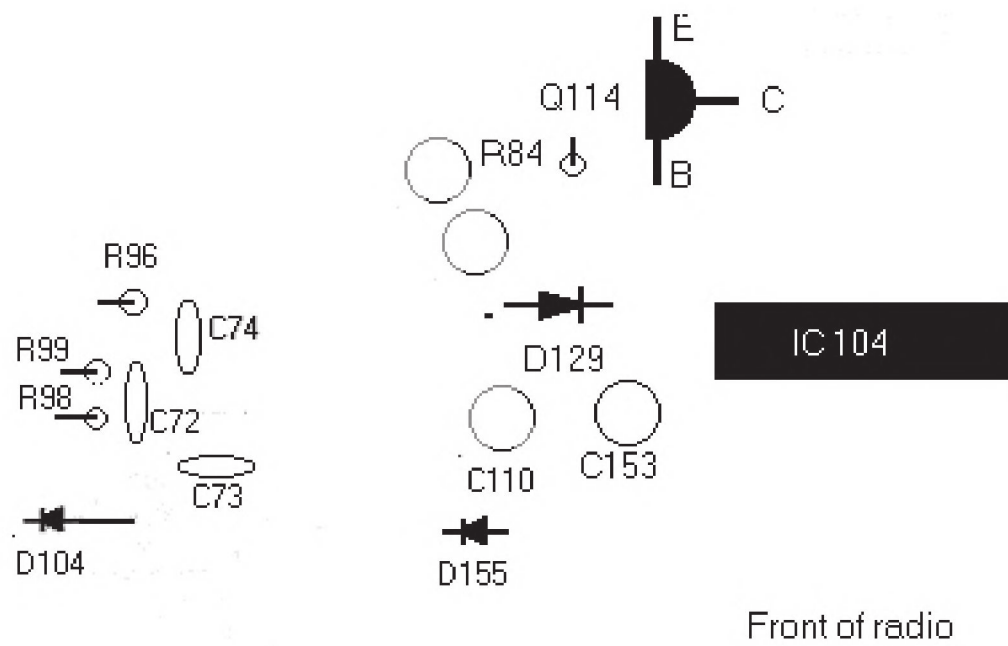

Adding an external meter to the HR2510

To add a needle type meter all you need to do is connect it to C302 on the Microprocessor.

If you are really interested, I suggest trying the CHIPSWITCH.

It gives you :

- 1) 30 memory channels, with temporary channel lockout and repeater offsets.**
- 2) Extended frequency coverage - 24.800 to 29.999 Mhz.**
- 3) Programmable Scan/Seek functions. Scan-This allows you to set a range of frequencies in any band, and even set the hold time during scans.**
Seek-This causes the radio to seek for active channels. both features are programmable from 5khz or 10 Khz steps.
- 4) Programmable channel up and down buttons. This is the ability to program the radios channel up and down button to change channels/freq. in any one of 5 different ways (5Khz, 10Khz, underlined digit, etc.).**
- 5) Programmable Mic channel up and down buttons. This allows programming the mic up/down buttons in any of 8 different ways.**
- 6) Split freq operation.**
- 7) programmable Xmit time out.(a built in QSO timer)**
- 8) Programmable transmit freq. range.**
- 9) Span underline cursor- allows 100Khz steps on the channel buttons, And the underlined digit can be changed with the Mic Buttons.**
- 10) Programmable button repeat.**
- 11) Programmable button beep duration.**
- 12) (in the 2600) RPTR button will toggle the xmit of CTCSS tones from a memory channel.**

This is a very versatile update. It does require the ability to remove the Microprocessor and solder in a new one. But it is fairly easy with a little soldering experience, and the right tools.

It comes with a complete manual and installation instructions. The cost from the manufacturer is now only \$49.95, and its available from copper electronics, if you want to go that way (I think Copper charges \$69.99).

Chipswitch can be ordered by Phone directly from the manufacurer, there address is:

CHIPSWITCH

4773 Sonoma Hwy. Suite 132

Santa Rosa, Ca. 95409-4269

Phone: (707) 539-0512 (answering machine for orders and info)

or you can visit their Website at: www.chipswitch.com

You can call them and order an information sheet prior to ordering the Chipswitch.


I reccommend this mod highly! Its easy and it does not require any new switches. It uses all the existing switches and buttons.

24 MHZ Broadband instructions for your HR2510

These instructions are to broadband your radio if you have the 24.000Mhz mod or the ChipSwitch installed.

MOD #1

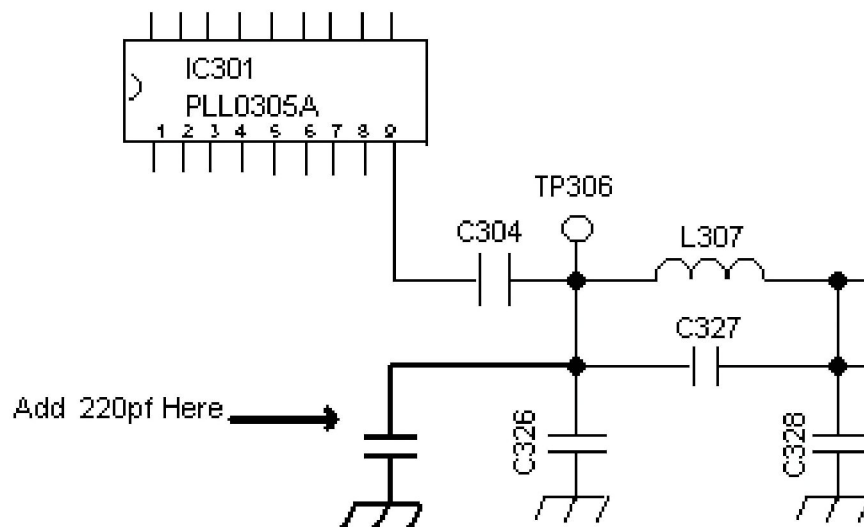1. Take the four screws out of the speaker cover on the radio.
2. With the radio upside down and the PLL board facing you, Remove the four screws in each corner of the pll board.
3. Loosen the four screws on the sides of the radio that hold the PLL tray in the radio. Loosen them all the way before they come completely out.
4. Pull the PLL board out towards you so the bottom of the PLL board is upside down.
5. Look at the diagram below and locate C304, C326, & C327. At the point where they connect together, you will place 1 leg of a 50V 220pf capacitor (Radio Shack P/N 272-124) and the other leg to



Ground of the board.

6. Check your work and make sure you did not short anything out and that you placed the capacitor in the right place.
7. Reassemble the PLL board and connect power to the radio.
8. Connect a watt meter and a dummy load to the antenna jack.
9. Put the radio on 29.500.Mhz and peak L310 for maximum output power.
10. Now put the radio on 25.500Mhz and peak L319 for maximim output power.
11. Reassemble your radio and your ready to go.


MOD #2 A simpler method...

Here is a simpler method of increasing the VCO coverage on the HR2510. If your HR2510 is Chipswitched, but doesn't lock on 12 Meters, this mod will take care of the problem without having to access the underside of the synth PCB.

Remove the four screws from the bottom cover and remove the cover.

On the PLL board locate L307 (TP306).

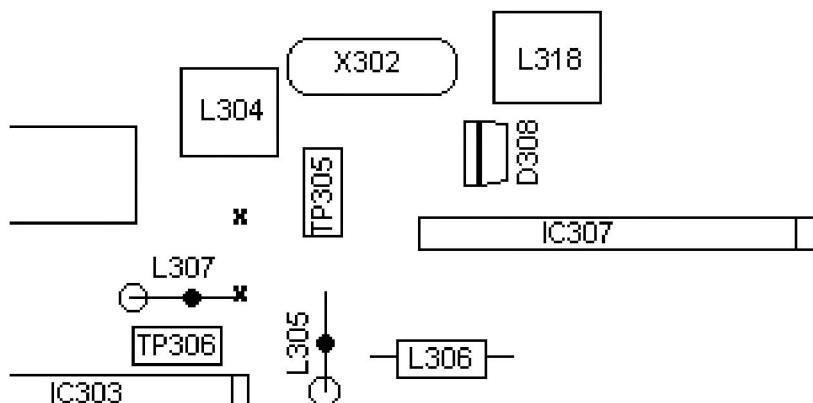Install a small ceramic capacitor between the long lead of L307 and ground. Any value between 180 and 220 picofarad (pf) will do. There is a convenient ground located just behind L307. this location is



The VCO range is extended by connecting a 180 to 220pf Capacitor between the two points marked " x ".

a plate-through hole (it looks like a shiny solder dot showing through the silk screening.)

The set should now lock from 24.800 to 29.900Mhz without further adjustment.

If you have access to a scope, the radio can easily be broadbanded for better performance in this new frequency range. to broadband, monitor the output at J311 and adjust L310 and L319 for equal output at the upper and lower limit of your operating range.

HR2510 Alignment Instructions - (Taken from the Uniden Service Manual)

Alignment of P.L.L. and Carrier Oscillator Portion

1. Test equipment required:

DC Power supply (13.8V)

DC Voltmeter

Dummy Load (50 Ohm)

Frequency Counter

Oscilloscope

2. Preperation for Alignment:

PA SW : Off

Mode SW : AM

RIT : Middle Position

TX SW : Off

3. Alignment Procedure:

	Preset to:	Adjust ment	Remarks
1	Mode : RX, AM SG : 28MHz	L315	Connect an oscilloscope to TP306. Adjust L315 For 6.200MHz +/- reading on the oscilloscope.
2	Ditto	L318	Connect the oscilloscpe to TP304. Adjust L318 for 38.695MHz +/- 20Hz reading on the oscilloscope.
3	Mode : RX, AM SG : 29.6999 MHz	L317	Connect a DC Voltmeter to TP303. Adjust L317 for 6.5 +/- 0.1V reading on the Dc Voltmeter.
4	Mode : RX, CW SG : 28 MHz	L117	Connect the oscilloscope to TP1. Adjust L117 for 10.6950MHz +/- 20Hz reading on the oscilloscope.
5	Mode : RX, LSB	L118	Adjust L118 for 10.6925MHz (-40Hz to +0Hz) reading on the oscilloscope).
6	Mode : RX, USB	L116	Adjust L116 for 10.6975MHz +/- 20 Hz reading on the oscilloscope.
7	Mode : RX, USB	VR111	Connect the oscilloscope to TP5. Adjust VR111 for 38.6975MHz +/- 20 Hz reading on the oscilloscope

Alignment of Transmitter Portion

1. Test equipment required:

DC Power supply (13.8V) more than 10A

AF S.S.G. AM FM (1kHz, 500Hz and 2400Hz)

RF VTVM

Oscilloscope

DC Ammeter

RF Power Meter

AF VTVM

Dummy Load (50 Ohm)

FM Linear Detector

2. Preperation for Alignment:

VR112 : Clockwise

PA SW : Off

VR113 : Counter Clockwise

Meter SW : RF

VR103 : Clockwise

MicGain SW : Off

SWR/CAL : Middle Position

TX SW : Off

Freq. : 28.000 MHz

3. Alignment Procedure:


	Preset to:	Adjustment	Remarks
1	Mode:USB No Mod.	VR112	Remove the B002(PB-100) from the Main PCB. Connect a DC Ammeter (+) to TP4, (-) to TP3. Adjust VR112 for 50mA reading on the DC Ammeter.
2	Ditto	VR113	Connect a DC Ammeter (+) to TP4, (-) to TP2. Adjust VR113 for 50 mA reading on DC Ammeter.
3	1mV Mod.	L111	Disconnect DC Ammeter. Reinstall the B002 to the Main PCB. Connect A RF Power meter to the ANT. jack. Connect a RF VTVM, an oscilloscope and a FM Linear Detector across a RF Dummy Load to the RF Power meter. Adjust L111 for maximum reading on the RF VTVM. During this step, set the AF oscillator so that the output is less than 20V. Repeat this two times.

4	30 mV Mod.	VR104	Adjust VR104 for 32.5V reading on the RF VTVM.
5	Ditto	VR106	Adjust VR106 so that the carrier leakage at USB and LSB becomes minimum and almost equal.
6	Mode: CW No Mod.	VR103	Connect a SW between Pin 8 and 9 of the ACC connector. With the SW turned on, adjust VR103 for 21W reading on the Power meter.
7	Mode: AM No Mod.	VR107	Adjust VR107 for 10W reading on the RF power meter.
8	Ditto	VR117	Adjust VR117 so that "9" LCD just lights on.
9	1 kHz, 30mV Modulation	VR114	Adjust VR114 to obtain the 85% negative reading on the oscilloscope.
10	1kHz, 1mV Modulation INDIC: MOD	VR115	Adjust VR115 so that "9" LCD just lights on.
11	Mode: FM 1kHz, 30mV Modulation	VR105	Adjust VR105 for +/- 3kHz deviation reading on the FM Linear Detector.
12	Mode: CW No Mod. Vol. : Max	VR116	Connect a AF VTVM across a dummy load (8 Ohm) between Pin 1 and Pin 2 of the ACC connector. With the SW turned on, adjust VR116 for 0.4V negative reading on the AF VTVM.


HR2510 Alignment and Test Point Layout

Refer to the HR2510 Alignment instructions

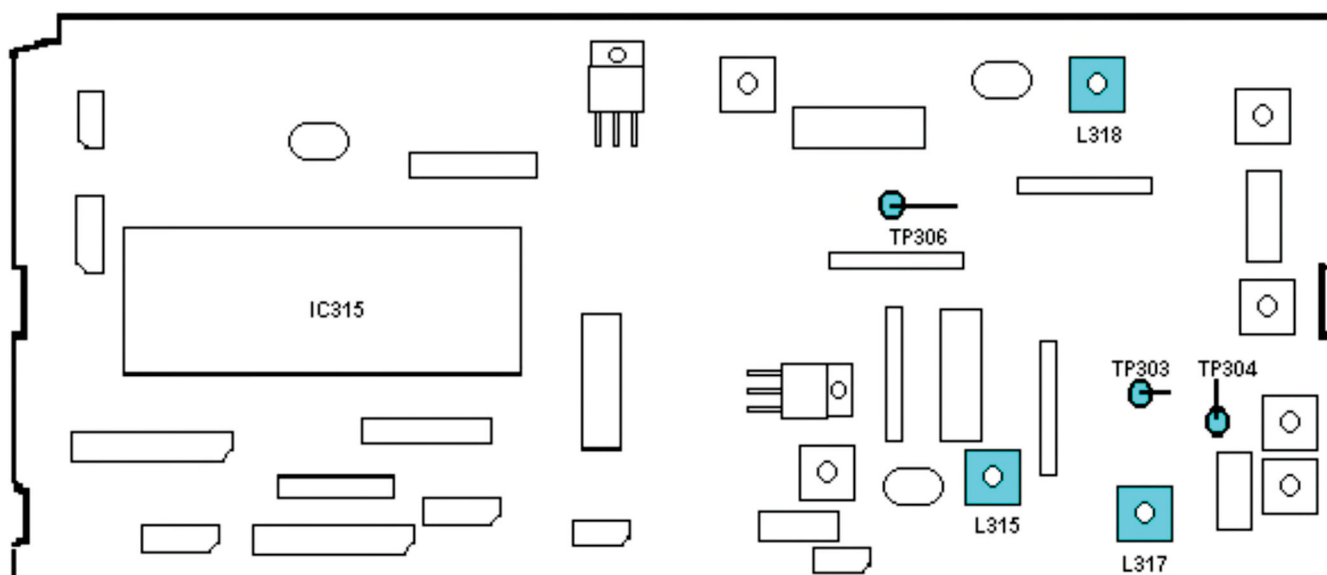
(The colors correspond to the adjustment procedure)



Synthesizer / Microprocessor / PLL PCB

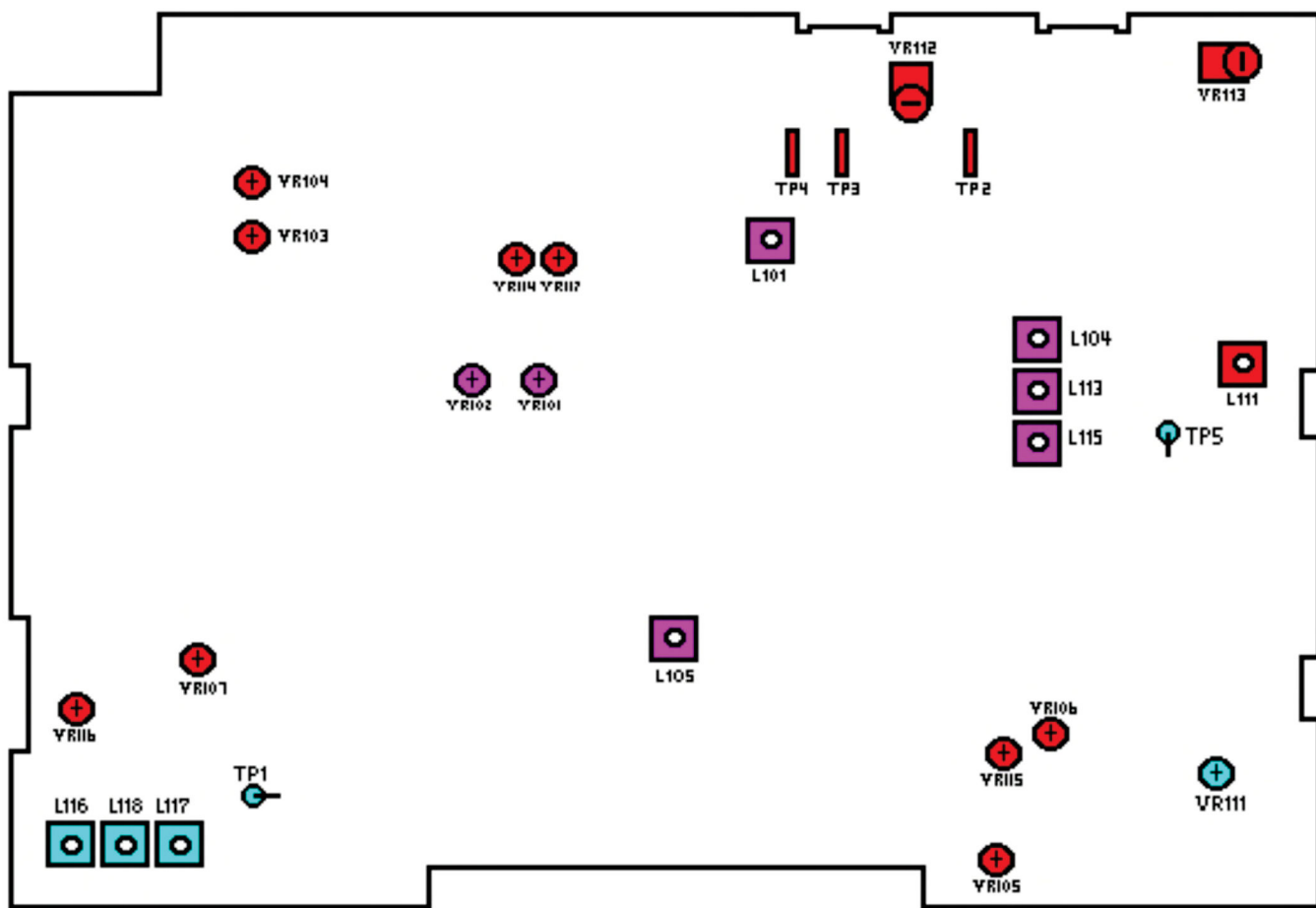

Main PCB

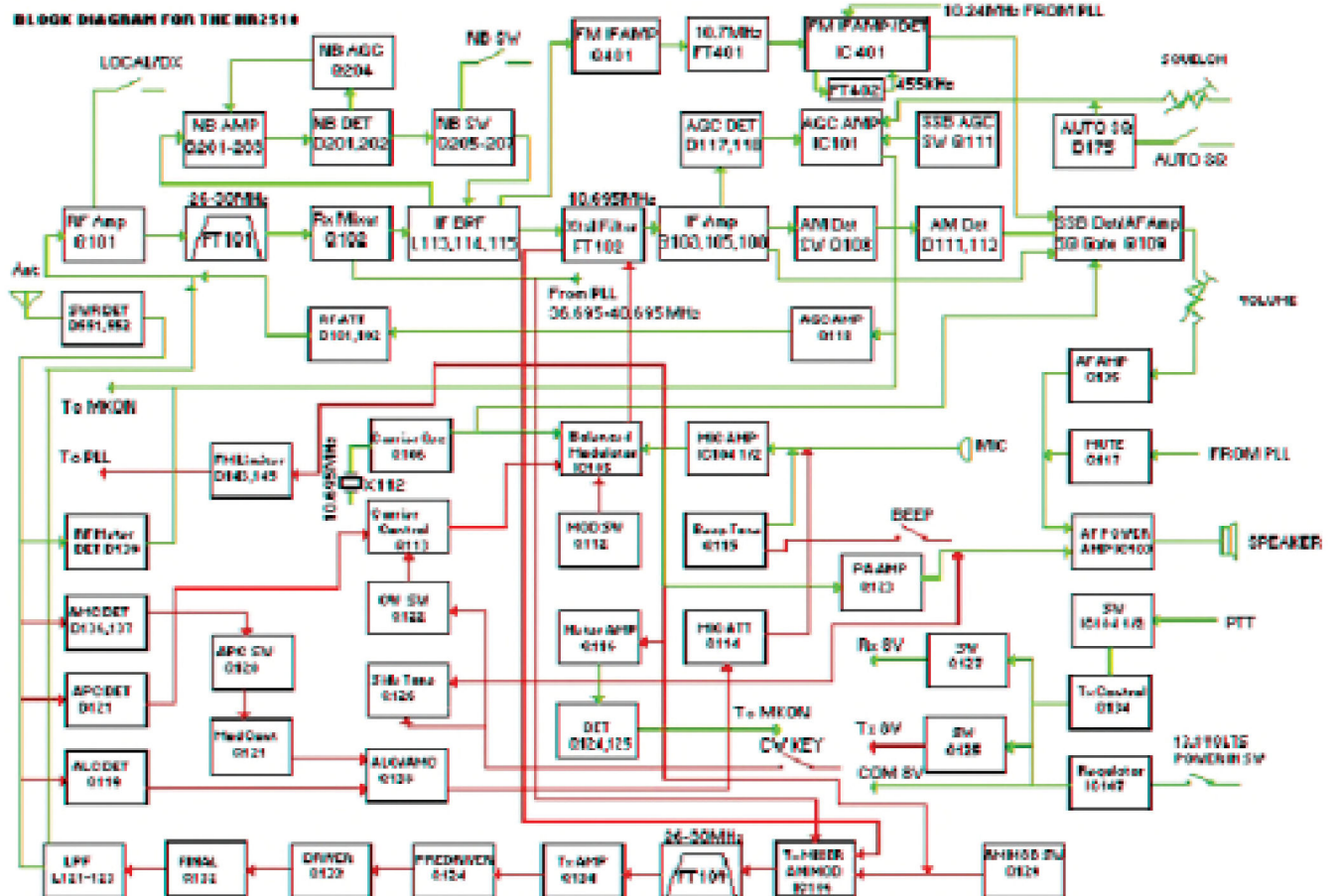

HR2510 Circuit Block Diagram

Microphone wiring

